

RLC step response

Design Parameters

Enter here the design parameters and component values

Input voltage $V_0 := 350 \text{ V}$

Series resistance $R_S := 0 \text{ } \Omega$


Parallel resistance $R_P := 1 \text{ M}\Omega$

Inductor value and ESR
 $L := 100 \text{ } \mu\text{H}$
 $R_L := 0.1 \text{ } \Omega$

Capacitor value, ESR and ESL
 $C := 440 \text{ } \mu\text{F}$
 $R_C := 0.3 \text{ } \Omega$
 $L_C := 0.1 \text{ } \mu\text{H}$

Plot time $T_{max} := 10 \text{ ms}$

Plot points $N := 10000$

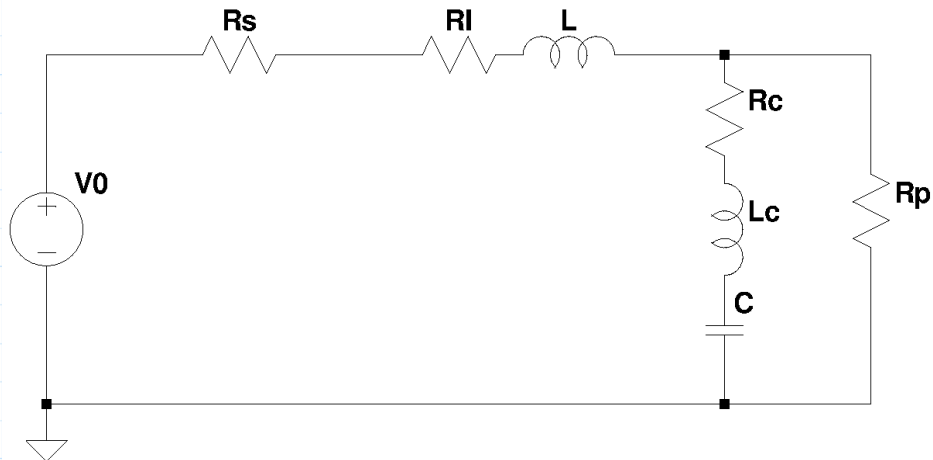

RLC step response

$$t := 0 \text{ } s, \frac{T_{max}}{N} .. T_{max}$$

ConstraintsGuess Values

$$I(0) = 0 \text{ } A$$

$$V(0) = 0 \text{ } V$$

$$V_C(0) = 0 \text{ } V$$

$$I_C(0) = 0 \text{ } A$$

$$I'(t) = \frac{1}{L} \cdot (V_0 - (R_L + R_S) \cdot I(t) - V(t))$$

$$V_C'(t) = \frac{1}{C} \cdot I_C(t)$$

$$V(t) = V_C(t) + R_C \cdot I_C(t) + L_C \cdot I_C'(t)$$

$$I(t) = I_C(t) + \frac{V(t)}{R_P}$$

Solver

$$\begin{bmatrix} I \\ V_C \\ V \\ I_C \end{bmatrix} := \text{odesolve} \left(\begin{bmatrix} I(t) \\ V_C(t) \\ V(t) \\ I_C(t) \end{bmatrix}, T_{max} \right)$$

$$I_{max} := \left\| \begin{array}{l} M \leftarrow 0 \text{ } A \\ \text{for } n \in 0 .. N \\ \quad \left\| \begin{array}{l} \text{if } I\left(n \cdot \frac{T_{max}}{N}\right) > M \\ \quad \left\| M \leftarrow I\left(n \cdot \frac{T_{max}}{N}\right) \end{array} \right\| \end{array} \right\| \right\| = 433.793 \text{ } A$$

RLC step response


$$V_{max} := \left\| \begin{array}{l} M \leftarrow 0 \text{ V} \\ \text{for } n \in 0..N \\ \quad \left\| \begin{array}{l} \text{if } V\left(n \cdot \frac{T_{max}}{N}\right) > M \\ \quad \left\| M \leftarrow V\left(n \cdot \frac{T_{max}}{N}\right) \end{array} \right. \end{array} \right\| = 453.515 \text{ V}$$

Peak values and plots


The following parameters are calculated from the previous ones. Do not edit them.

Maximum current in the inductor $I_{max} = 433.8 \text{ A}$

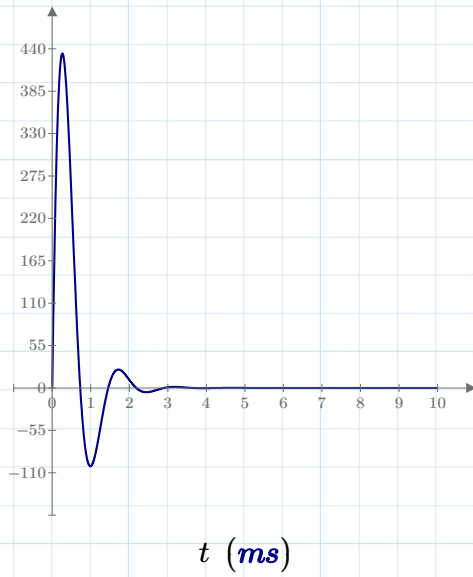Maximum voltage on the capacitor $V_{max} = 453.5 \text{ V}$



RLC step response

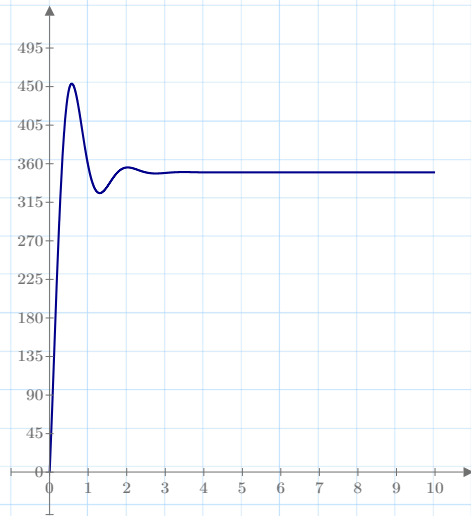

$V(t)$ (V)

t (ms)