

MNA Solver

☑ MNA STAMPS

☑ BodePlot

☑ RLC Examples


Short hands:

$$V(n) := \left| MNA(\chi, MNA_{AC}) \right|_4 n$$

$$\chi' := \left| \chi \right|_{[1 \dots \text{rows}(\chi)][1 \dots 2]}$$

$$Sym(n) := \left| \frac{MNA(\chi', MNA_{AC})}{V_{in}} \right|_4 n$$

Exact transfer fuction (voltage gain)

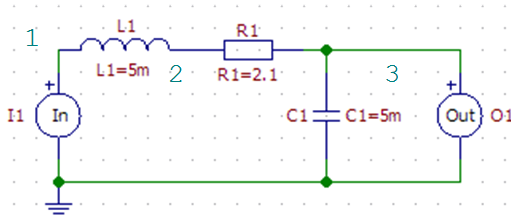

$$\chi := \begin{bmatrix} V_{in} & \begin{bmatrix} 1 & 0 \\ L & \begin{bmatrix} 1 & 2 \\ 0 & 3 \end{bmatrix} \\ C & \begin{bmatrix} 0 & 3 \\ 2 & 3 \end{bmatrix} \\ R & R \end{bmatrix} & V_{in} \\ 5 \text{ mH} \\ 5 \text{ mF} \\ R \end{bmatrix}$$

$$H(s) := \frac{V(3)}{V_{in}}$$

$$Sym(3) = \frac{R}{(1 + s \cdot C \cdot R) \cdot (R + s \cdot L) - s \cdot L}$$





Plots are:

BodeMag BodePhase
ZP Plot Nyquist Nichols

$R := 2.1 \Omega$
 $\text{Bode}_1 := \text{logspace}(1, 4) \text{ Hz}$
 $\Pi := \text{Bode}(H(s\#))$



Big losses: R=2.1Ω




65536				Y
32768				
0			XX	X
-32768				
-2048		-1024		0

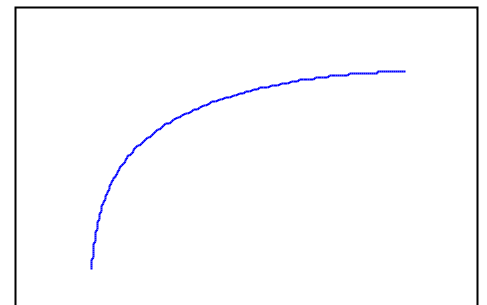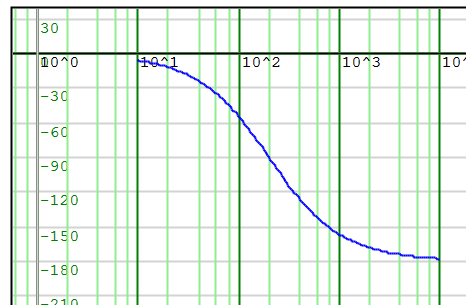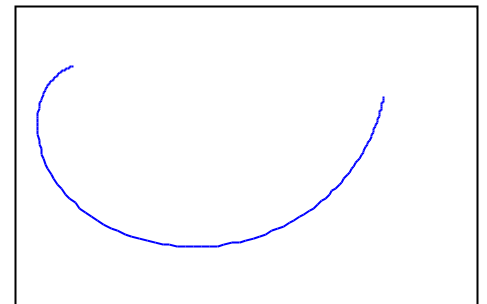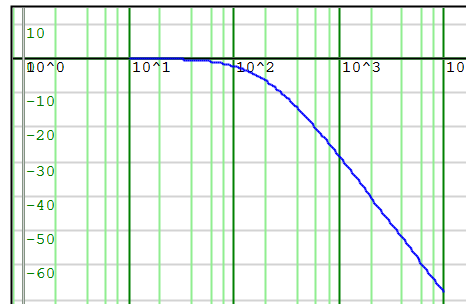


$R := 0.51 \Omega$
 $\text{Bode}_1 := \text{logspace}(1, 4) \text{ Hz}$
 $\Pi := \text{Bode}(H(s\#))$

Small losses: R=0.51Ω

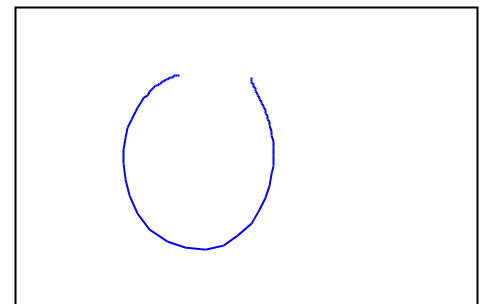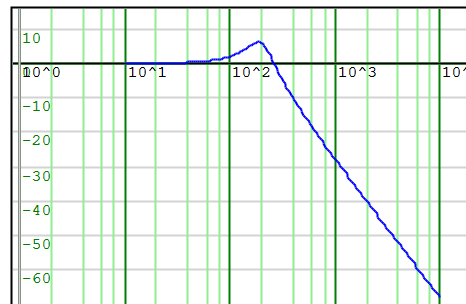

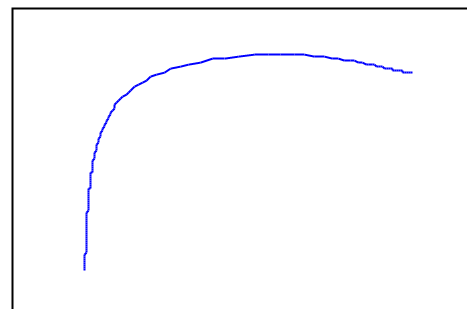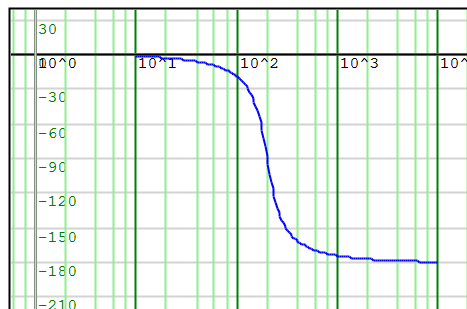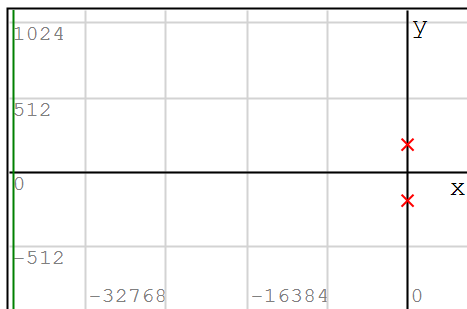

Parallel resonant circuit

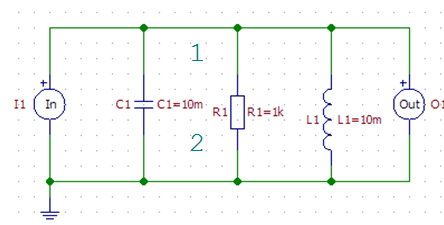






Clear(R)=1

$$\chi := \begin{bmatrix} V_{in} & [1 \ 0] & V_{in} \\ L & [1 \ 2] & 10 \text{ mH} \\ C & [0 \ 3] & 10 \text{ mF} \\ R & [2 \ 3] & 1 \ \Omega \end{bmatrix}$$


$$H(s) := \frac{V(2)}{V_{in}}$$

$$Sym(2) = \frac{R \cdot (1 + s \cdot C \cdot R)}{(1 + s \cdot C \cdot R) \cdot (R + s \cdot L) - s \cdot L}$$

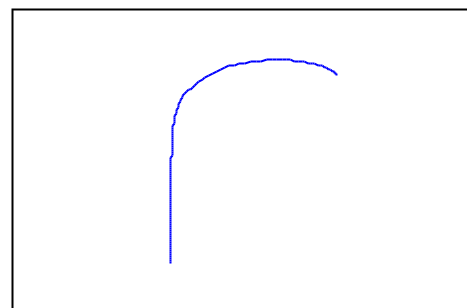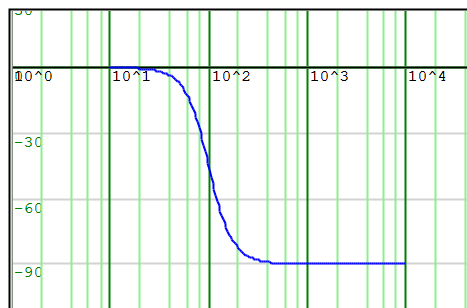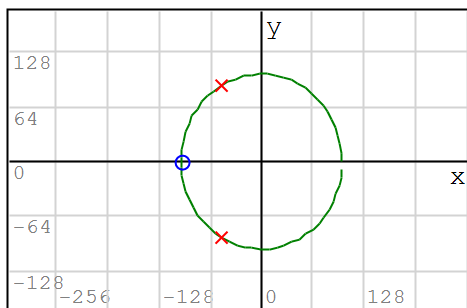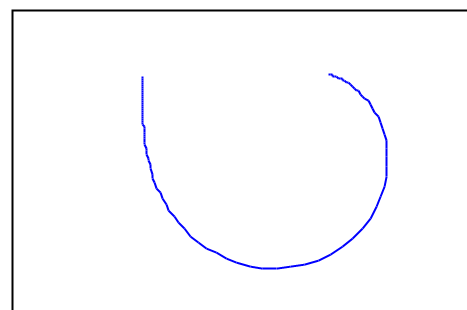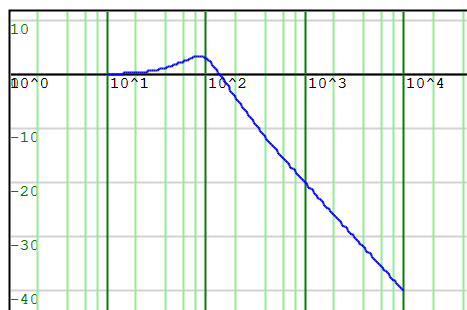$\{ \text{Bode}_1 := \text{logspace}(1, 4) \text{ Hz}$
 $\Pi := \text{Bode}(H(s\#))$



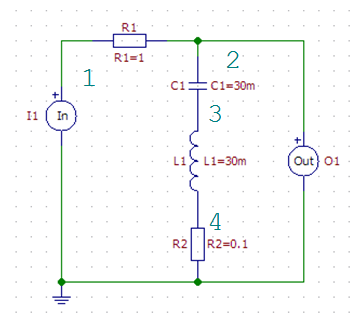Band resistor with serial resonant circuit








$$\chi := \begin{bmatrix} V_{in} & [1 \ 0] & V_{in} \\ L & [3 \ 4] & 30 \text{ mH} \\ C & [2 \ 3] & 30 \text{ mF} \\ R_1 & [1 \ 2] & 1 \ \Omega \\ R_2 & [0 \ 4] & 0.1 \ \Omega \end{bmatrix}$$

$$H(s) := \frac{V(2)}{V_{in}}$$

$$Sym(2) = \frac{-R_2 + (1 + s^2 \cdot C \cdot L) \cdot (R_2 + s \cdot L)}{-(1 + s \cdot C \cdot R_1) \cdot R_2 + (R_2 + s \cdot L) \cdot ((1 + s^2 \cdot C \cdot L) \cdot (1 + s \cdot C \cdot R_1) - s^3 \cdot C^2 \cdot R_1 \cdot L)}$$
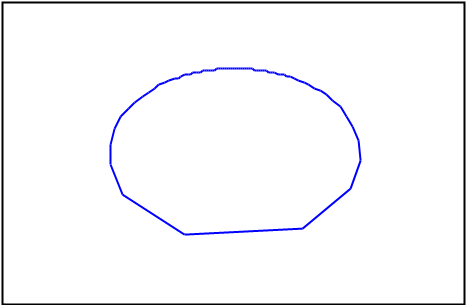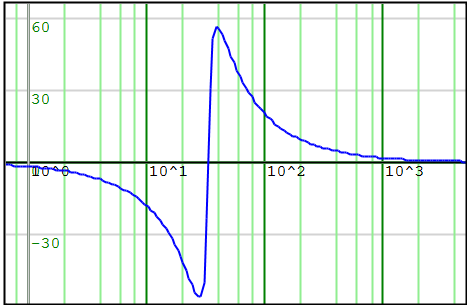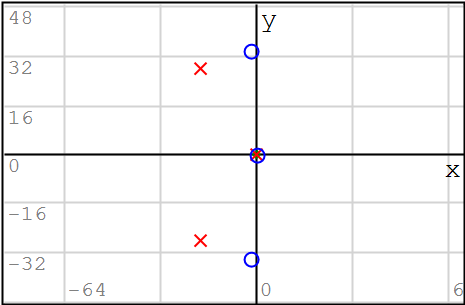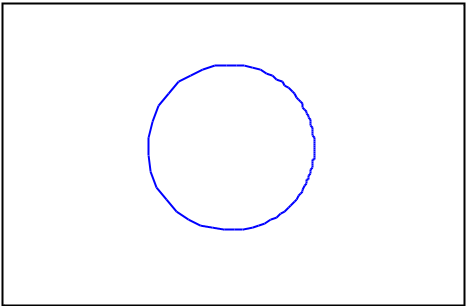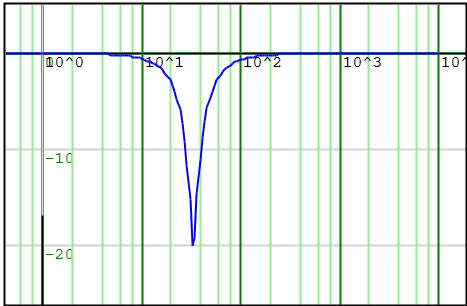
```
{ Bode_1 := logspace (-1, 4) Hz
  Π := Bode (H (s#)) }
```



Alvaro