


Ideal Atwood Machine.

$$eq := \begin{cases} m_1 \cdot g - T = m_1 \cdot a & \text{equation for m.1} \\ T - m_2 \cdot g = m_2 \cdot a & \text{equation for m.2} \end{cases} \quad \begin{cases} T := isol(eq_1, T) \\ a := isol(eq_2, a) \end{cases}$$

$$T = \frac{2 \cdot m_1 \cdot m_2 \cdot g}{m_1 + m_2} \quad a = \frac{g \cdot (m_1 - m_2)}{m_1 + m_2}$$

Numerical example
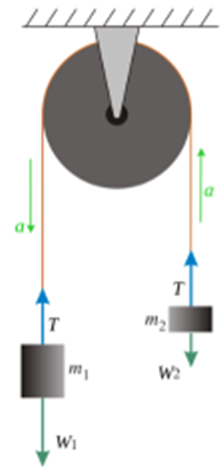
$$\begin{cases} m_1 := 4 \text{ kg} & T = 6 \text{ kgf} \\ m_2 := 12 \text{ kg} & a = -0.5 g_e \\ g := g_e \end{cases}$$



Atwood Machine with pulley with inertia and friction.

$$eq := \begin{cases} m_1 \cdot g - T_1 = m_1 \cdot a \\ T_2 - m_2 \cdot g = m_2 \cdot a \\ (T_1 - T_2) \cdot r - \tau_f = I \cdot \alpha \\ a = \alpha \cdot r \end{cases} \quad \begin{cases} T_1 := isol(eq_1, T_1) \\ T_2 := isol(eq_2, T_2) \\ \alpha := isol(eq_3, \alpha) \end{cases} \quad \text{No solve for a yet}$$

equation for pulley
Non-sleep condition

$$T_1 = -m_1 \cdot (-g + a) \quad T_2 = m_2 \cdot (g + a)$$

$$\alpha = -\frac{\tau_f + (m_1 \cdot (-g + a) + m_2 \cdot (g + a)) \cdot r}{I} \quad a := isol(eq_4, a) = -\frac{(\tau_f + g \cdot (-m_1 + m_2) \cdot r) \cdot r}{I + r^2 \cdot (m_1 + m_2)}$$

If $\begin{cases} \tau_f := 0 \\ I := 0 \end{cases}$ we recover the ideal case

$$T_1 = \frac{2 \cdot m_1 \cdot m_2 \cdot g}{m_1 + m_2} \quad T_2 = \frac{2 \cdot m_2 \cdot m_1 \cdot g}{m_1 + m_2} \quad a = -\frac{g \cdot (-m_1 + m_2)}{m_1 + m_2}$$


Numerical example

$$\begin{cases} m_1 := 4 \text{ kg} & r := 12 \text{ cm} & \text{Pulley radius} & T_1 = 5.9901 \text{ kgf} \\ m_2 := 12 \text{ kg} & M := 0.5 \text{ kg} & \text{mass} & T_2 = 6.0296 \text{ kgf} \\ g := g_e & I := 0.5 \cdot M \cdot r^2 & \text{Inertia} & a = -0.4975 g_e \\ & \tau_f := 0.1 \text{ N m} & \text{frictional torque} & \end{cases}$$

Almost the same values for the ideal case, for $\tau.f$ small.

Parallel Capacitors
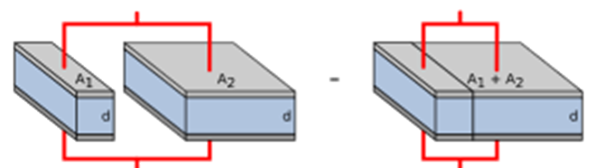
$$eq := \begin{cases} Q = q_1 + q_2 \\ q_1 = C_1 \cdot V \\ q_2 = C_2 \cdot V \\ Q = V \cdot C_{eq} \end{cases} \quad \begin{cases} q_1 := isol(eq_1, q_1) \\ q_2 := isol(eq_2, q_2) \\ V := isol(eq_3, V) \\ C_{eq} := isol(eq_4, C_{eq}) \end{cases}$$




$$q_1 = \frac{C_1 \cdot Q}{C_1 + C_2} \quad q_2 = \frac{Q \cdot C_2}{C_1 + C_2} \quad V = \frac{Q}{C_1 + C_2}$$

$$C_{eq} = C_2 + C_1$$

Series Capacitors
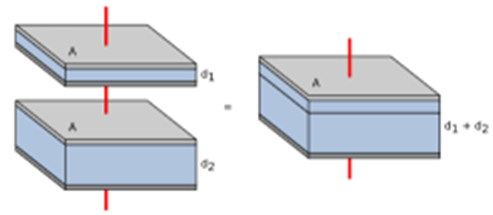
$$eq := \begin{cases} Q = V_1 \cdot C_1 \\ Q = V_2 \cdot C_2 \\ V = V_1 + V_2 \\ Q = V \cdot C_{eq} \end{cases} \quad \begin{cases} Q := isol(eq_1, Q) \\ V_1 := isol(eq_2, V_1) \\ V_2 := isol(eq_3, V_2) \\ C_{eq} := isol(eq_4, C_{eq}) \end{cases}$$



$$V_1 = \frac{V \cdot C_2}{C_1 + C_2} \quad V_2 = \frac{V \cdot C_1}{C_1 + C_2} \quad Q = \frac{V \cdot C_1 \cdot C_2}{C_1 + C_2}$$

$$C_{eq} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

Alvaro