

MNA Solver

⊕—Numerical Inverse Laplace Transform—

⊕—MNA STAMPS—


⊖—OpAmp Integrator—

OpAmp integrator

Shorthands: $V_{SOL} := MNA \left(\chi, MNA_{AC} \right)_4$

$v_o(t) := \left| ILap \left(V_o(s), t, t_i, t_e, 16 \right) \right|$
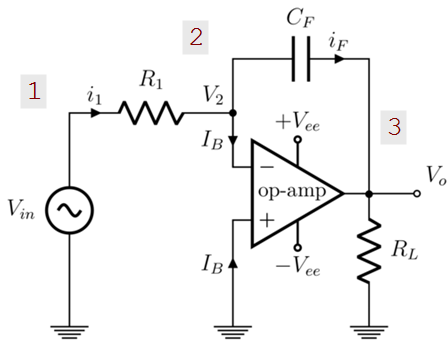
$$\Pi := \begin{cases} v_i(x \ s) \cdot t_i \leq x \ s \leq t_e \\ v_o(x \ s) \cdot t_i \leq x \ s \leq t_e \\ v_{os}(x \ s) \cdot t_i \leq x \ s \leq t_e \end{cases}$$



Ideal integrator

$$\chi := \begin{bmatrix} V_i(s) & [1 & 0] \\ R_1 & [1 & 2] \\ R_L & [0 & 3] \\ C_F & [2 & 3] \\ 0 & [0 & 3 & 2] \end{bmatrix}$$

Symbolic solution in freq domain

$$V_o(s) := V_{SOL} = -\frac{V_i(s)}{s \cdot C_F \cdot R_1}$$

Symbolic solution in time domain

$$v_{os}(t) := -\frac{1}{C_F \cdot R_1} \cdot \int_{t_i}^t v_i(\tau \ s) d\tau$$

Numerical values

$$\begin{bmatrix} t_i & t_e \end{bmatrix} := \begin{bmatrix} 0 \ s & 300 \ ms \end{bmatrix} \quad f := 8 \ Hz \quad V_o := 150 \ mV$$

$$\omega := 2 \cdot \pi \cdot f = 50.2655 \ Hz$$


$$R_1 := 220 \ k\Omega \quad R_L := 320 \ \Omega \quad C_F := 200 \ nF$$

$$T := \frac{1}{f} = 0.125 \ s$$

$$\begin{cases} v_i(t) := V_o \cdot \text{sign}(\sin(\omega \cdot t)) \\ V_i(s) := \frac{V_o}{s} \cdot TH\left(\frac{s \cdot T}{4}\right) \end{cases}$$


Pulse train input

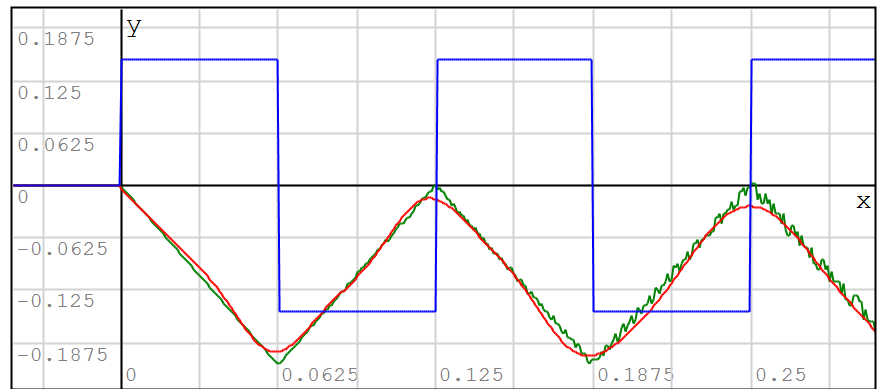- blue: input signal
- red: ILap solution
- green: integrate solution




$$\begin{cases} v_i(t) := V_o \cdot \sin(\omega \cdot t) \\ V_i(s) := V_o \cdot \frac{\omega}{s^2 + \omega^2} \end{cases}$$

Sinusoidal input

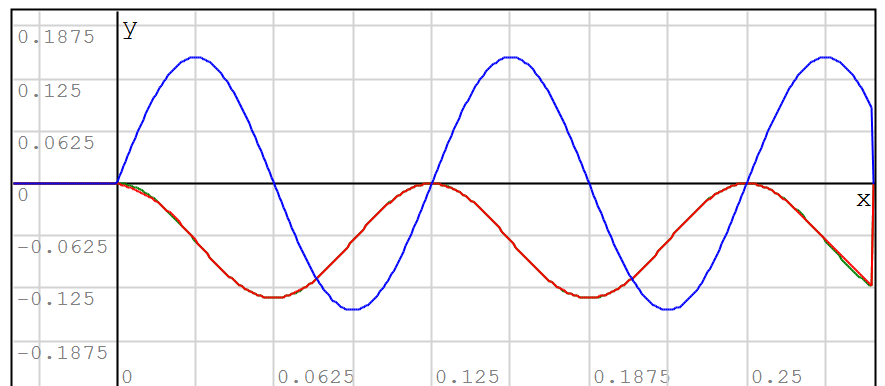

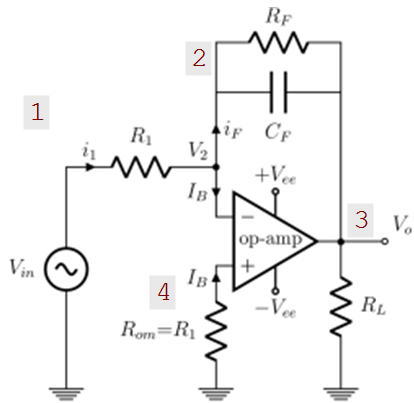Clear($V_i(s), V_o, T, \omega, R_1, R_L, C_F$)=1



Real integrator

Symbolic solution in freq domain

$$\chi := \begin{bmatrix} V_i(s) & [1 & 0] \\ R_1 & [1 & 2] \\ R_L & [0 & 3] \\ C_F & [2 & 3] \\ 0 & [4 & 3 & 2] \\ R_F & [2 & 3] \\ R_1 & [0 & 4] \end{bmatrix}$$

$$V_o(s) := V_{sol} = - \frac{V_i(s) \cdot R_F}{(1 + s \cdot C_F \cdot R_F) \cdot R_1}$$

Symbolic solution in time domain

Can't find a general explicit expression.

$$\text{maple}\left(\text{invlaplace}\left(V_o(s), s, t\right)\right) = - \frac{R_F \cdot \text{invlaplace}\left(\frac{V_i(s)}{1 + s \cdot C_F \cdot R_F}, s, t\right)}{R_1}$$

Search a particular symbolic solution

Pulse train

$$V_i(s) := \frac{V_o}{s} \cdot \tanh\left(\frac{s \cdot T}{4}\right)$$

$$v_{pulse} := \text{maple}\left(\text{invlaplace}\left(V_o(s), s, t\right)\right)$$

$$v_{pulse} = - \frac{V_o \cdot R_F \cdot \left((-1) \cdot \left(-1 + \text{ceil}\left(\frac{2 \cdot t}{T}\right) \right) - C_F \cdot R_F \cdot \text{invlaplace}\left(\frac{\tanh\left(\frac{s \cdot T}{4}\right)}{1 + s \cdot C_F \cdot R_F}, s, t\right) \right)}{R_1}$$

Fails, take $v_{pulse} := 0$

Sinusoidal

$$V_i(s) := V_o \cdot \frac{\omega}{s^2 + \omega^2}$$

$$v_{sin} := \text{maple}\left(\text{invlaplace}\left(V_o(s), s, t\right)\right)$$

$$v_{sin} = - \frac{V_o \cdot R_F \cdot \left(-C_F \cdot R_F \cdot \cos(\omega \cdot t) \cdot \omega + \sin(\omega \cdot t) + C_F \cdot R_F \cdot \exp\left(-\frac{t}{C_F \cdot R_F}\right) \cdot \omega \right)}{R_1 \cdot \left(1 + C_F^2 \cdot R_F^2 \cdot \omega^2 \right)}$$

It's OK

Numerical values

$$\begin{bmatrix} t_i & t_e \end{bmatrix} := \begin{bmatrix} 0 & 300 \text{ ms} \end{bmatrix} \quad f := 8 \text{ Hz} \quad V_o := 150 \text{ mV}$$

$$R_F := 250 \text{ k}\Omega$$


$$R_1 := 220 \text{ k}\Omega \quad R_L := 320 \text{ }\Omega \quad C_F := 200 \text{ nF}$$

$$R_{om} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_F} + \frac{1}{R_L}} = 0.3191 \text{ k}\Omega$$

$$\omega := 2 \cdot \pi \cdot f = 50.2655 \text{ Hz} \quad T := \frac{1}{f} = 0.125 \text{ s}$$


$$\begin{cases} v_i(t) := V_o \cdot \text{sign}(\sin(\omega \cdot t)) \\ V_i(s) := \frac{V_o}{s} \cdot TH\left(\frac{s \cdot T}{4}\right) \\ v_{os}(t) := 0 \end{cases}$$

Pulse train input

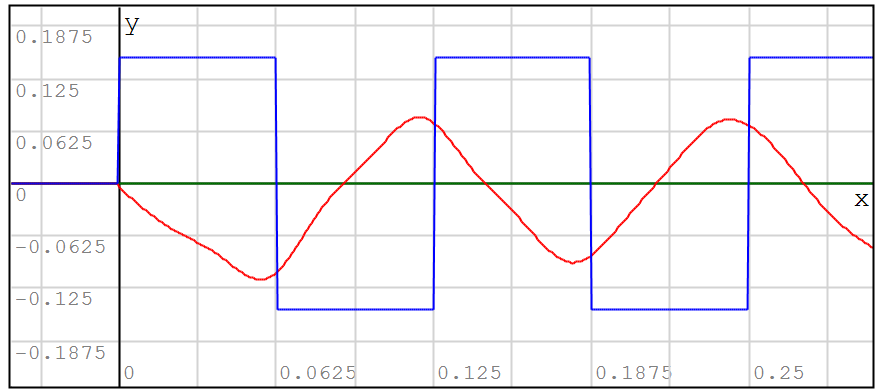

$$\begin{cases} v_i(t) := V_o \cdot \sin(\omega \cdot t) \\ V_i(s) := V_o \cdot \frac{\omega}{s^2 + \omega^2} \\ v_{os}(t) := v_{sin} \end{cases}$$


Sinusoidal input

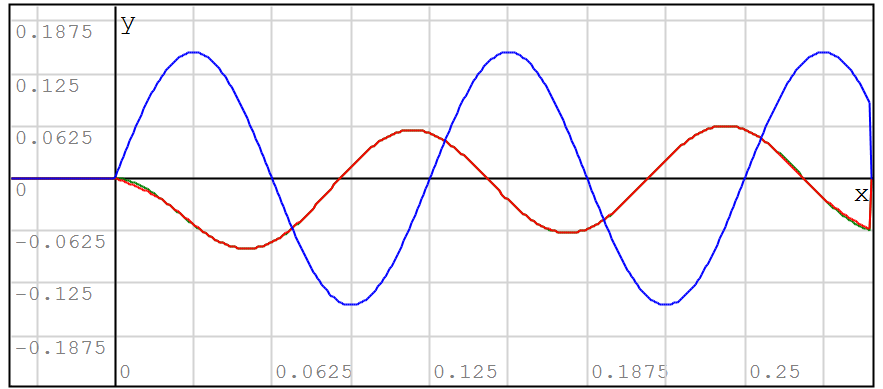

Summary of basic op amp circuits

$$\text{Clear}(V_i, R_1, \chi) = 1$$

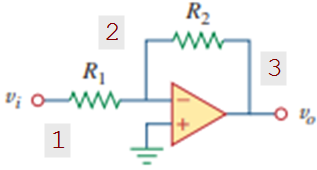
$$V_{sol} := \text{MNA}(\chi, \text{MNA}_{AC})_4$$



Inverter
amplifier

$$\chi := \begin{bmatrix} V_i & [1 & 0] \\ R_1 & [1 & 2] \\ R_2 & [2 & 3] \\ O & [0 & 3 & 2] \end{bmatrix}$$

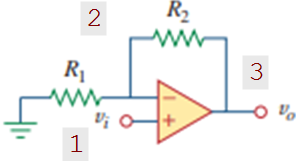
$$V_o := V_{sol}_3 \quad V_o = -\frac{V_i \cdot R_2}{R_1}$$



Noninverter
amplifier

$$\chi := \begin{bmatrix} V_i & [1 & 0] \\ R_1 & [0 & 2] \\ R_2 & [2 & 3] \\ O & [1 & 3 & 2] \end{bmatrix}$$

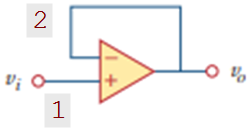
$$V_o := V_{sol}_3 \quad V_o = \frac{(R_1 + R_2) \cdot V_i}{R_1}$$



Voltage
Follower

$$\chi := \begin{bmatrix} V_i & [1 & 0] \\ O & [1 & 2 & 2] \end{bmatrix}$$

$$V_o := V_{sol}_2 \quad V_o = V_i$$

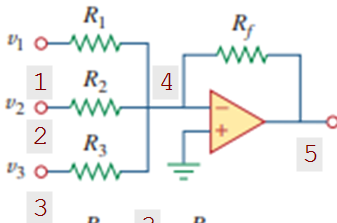


Summer

$$\chi := \begin{bmatrix} V_1 & [1 & 0] \\ V_2 & [2 & 0] \\ V_3 & [3 & 0] \\ R_1 & [1 & 4] \\ R_2 & [2 & 4] \\ R_3 & [3 & 4] \\ R_f & [4 & 5] \\ O & [0 & 5 & 4] \end{bmatrix}$$

$$V_o := V_{sol}_5$$
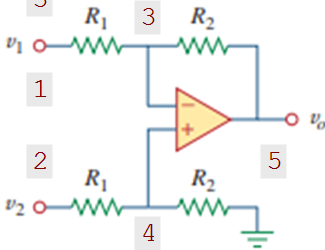
$$V_o = -\frac{R_f \cdot \left((V_1 \cdot R_2 + V_2 \cdot R_1) \cdot R_3 + V_3 \cdot R_2 \cdot R_1 \right)}{R_3 \cdot R_2 \cdot R_1}$$



Difference
Amplifier

$$\chi := \begin{bmatrix} V_1 & [1 & 0] \\ V_2 & [2 & 0] \\ R_1 & [3 & 1] \\ R_1 & [4 & 2] \\ R_2 & [0 & 4] \\ R_2 & [3 & 5] \\ O & [4 & 5 & 3] \end{bmatrix}$$

$$V_o := V_{sol}_5 \quad V_o = \frac{R_2 \cdot (-V_1 + V_2)}{R_1}$$