

MNA Solver


☐ Include

☐ RLC Examples

Short hands: $V(n) := \left| MNA(\chi, MNA_{AC}) \right|_n$

$Sym(n) := \left| \frac{MNA(\chi', MNA_{AC})}{V_{in}} \right|_n$ Exact transfer function (voltage gain)

$\chi' := \left| \chi \right|_{[1..rows(\chi)][1..2]}$

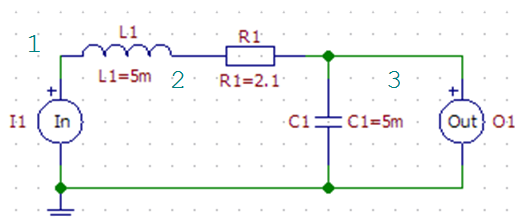

$$\chi := \begin{bmatrix} V_{in} & \begin{bmatrix} 1 & 0 \end{bmatrix} & V_{in} \\ L & \begin{bmatrix} 1 & 2 \end{bmatrix} & 5 \text{ mH} \\ C & \begin{bmatrix} 0 & 3 \end{bmatrix} & 5 \text{ mF} \\ R & \begin{bmatrix} 2 & 3 \end{bmatrix} & R \end{bmatrix}$$




$$H(s) := \frac{V(3)}{V_{in}}$$

$$Sym(3) = \frac{R}{(1 + s \cdot C \cdot R) \cdot (R + s \cdot L) - s \cdot L}$$




Plots are:

ZP Plot BodeMag BodePhase
Nyquist Nichols

$R := 2.1 \Omega$
 $Code_1 := \text{logspace}(1, 4) \text{ Hz}$
 $\Pi := \text{Bode}(H(s\#))$

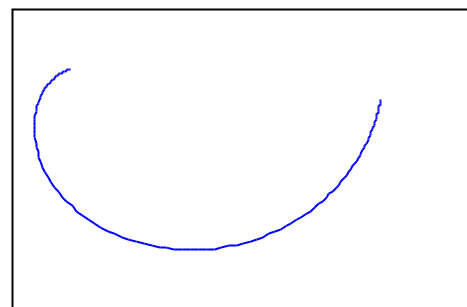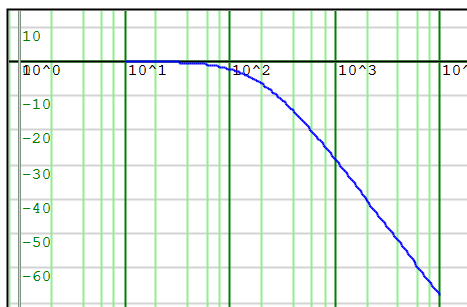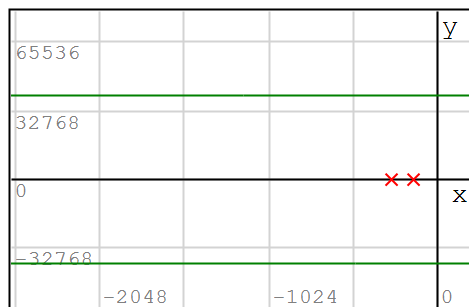
Big losses: $R=2.1\Omega$ 

$R := 0.51 \Omega$
 $Code_1 := \text{logspace}(1, 4) \text{ Hz}$
 $\Pi := \text{Bode}(H(s\#))$

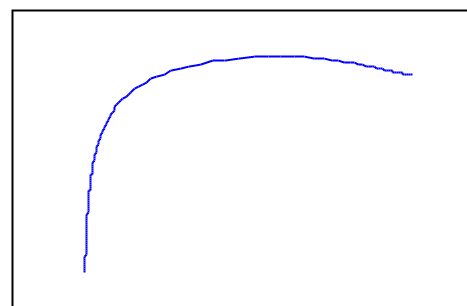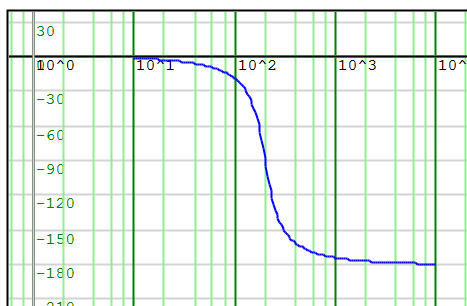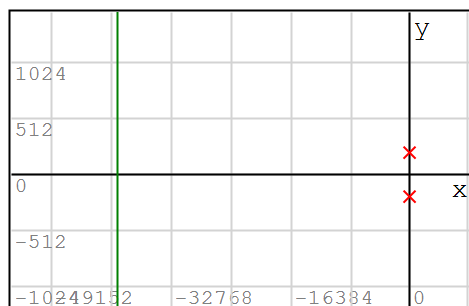Small losses: $R=0.51\Omega$ 

Parallel resonant circuit

Clear(R)=1





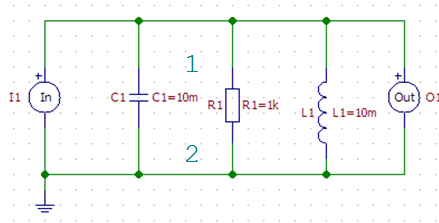


$$\chi := \begin{bmatrix} V_{in} & \begin{bmatrix} 1 & 0 \end{bmatrix} & V_{in} \\ L & \begin{bmatrix} 1 & 2 \end{bmatrix} & 10 \text{ mH} \\ C & \begin{bmatrix} 0 & 3 \end{bmatrix} & 10 \text{ mF} \\ R & \begin{bmatrix} 2 & 3 \end{bmatrix} & 1 \Omega \end{bmatrix}$$


$$H(s) := \frac{V(2)}{V_{in}}$$

$$\text{Sym}(2) = \frac{R \cdot (1 + s \cdot C \cdot R)}{(1 + s \cdot C \cdot R) \cdot (R + s \cdot L) - s \cdot L}$$

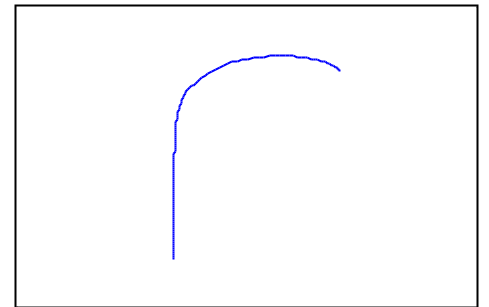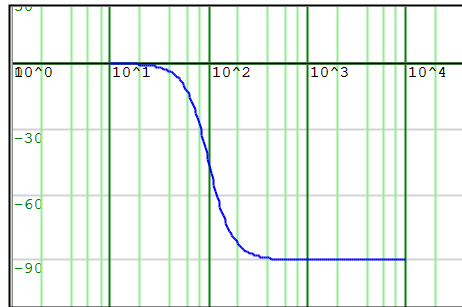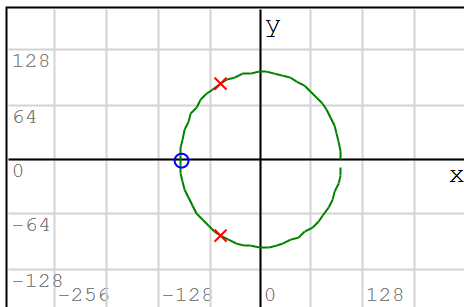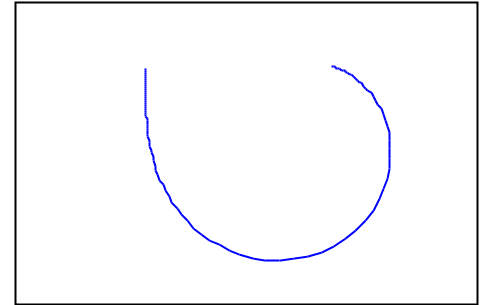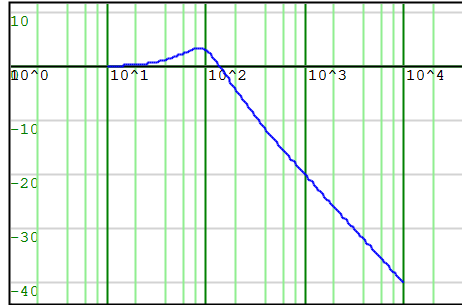$\text{Bode}_1 := \text{logspace}(1, 4) \text{ Hz}$
 $\Pi := \text{Bode}(H(s\#))$



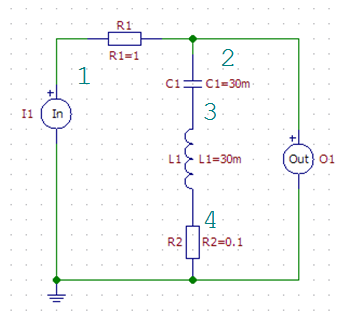Band resistor with serial resonant circuit








$$\chi := \begin{bmatrix} V_{in} & \begin{bmatrix} 1 & 0 \end{bmatrix} & V_{in} \\ L & \begin{bmatrix} 3 & 4 \end{bmatrix} & 30 \text{ mH} \\ C & \begin{bmatrix} 2 & 3 \end{bmatrix} & 30 \text{ mF} \\ R_1 & \begin{bmatrix} 1 & 2 \end{bmatrix} & 1 \Omega \\ R_2 & \begin{bmatrix} 0 & 4 \end{bmatrix} & 0.1 \Omega \end{bmatrix}$$

$$H(s) := \frac{V(2)}{V_{in}}$$

$$\text{Sym}(2) = \frac{-R_2 + (1 + s^2 \cdot C \cdot L) \cdot (R_2 + s \cdot L)}{-(1 + s \cdot C \cdot R_1) \cdot R_2 + (R_2 + s \cdot L) \cdot ((1 + s^2 \cdot C \cdot L) \cdot (1 + s \cdot C \cdot R_1) - s^3 \cdot C^2 \cdot R_1 \cdot L)}$$

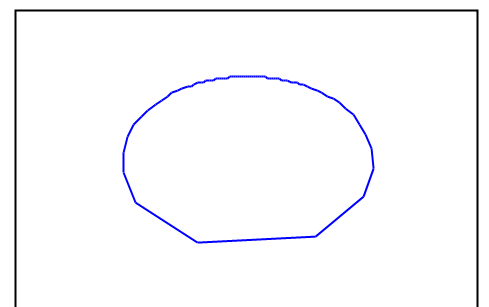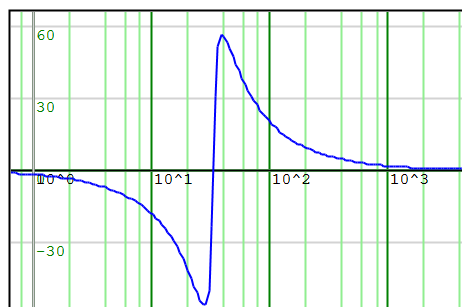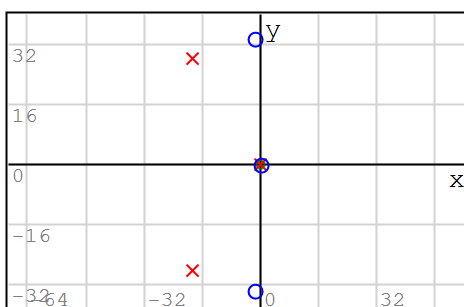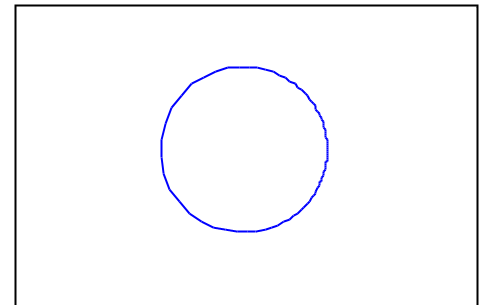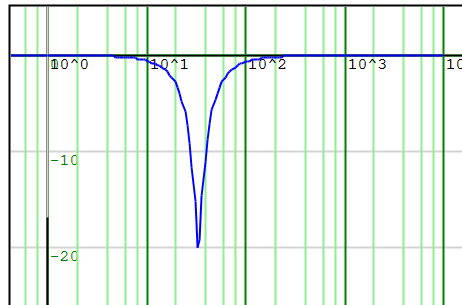$\text{Bode}_1 := \text{logspace}(-1, 4) \text{ Hz}$
 $\Pi := \text{Bode}(H(s\#))$



Alvaro